

TDC_Lab_4. Memory design using VHDL

4.1. Modeling RAM memory with VHDL

RAM memory

- Create a new Project, **Project_23**, and add a VHDL file to describe a generic Write-First RAM memory. (Synchronous Write and Read)
- Set the generics **ADDR_WIDTH** to 2 bits ($2^{**}M$) and **DATA_WIDTH** to 8 bits (N).
- Test the circuit onto Nexys4, use switches and LED.
- Firstly write some data in several address, then read the data.

Project's name: **Project_23**

Entity's name: "RAM_WF_MxN"

Inputs: DATA_RAM_i, ADDR_RAM_i, WE_i, CLK_i

Outputs: DATA_RAM_o

4.2. DATAPATH and RAM

Adding a RAM to DATAPATH

P24_DATAPATH_0_RAM


Vivado allows copying projects. Now, copy the P22_Datapath_0_ALU_RA_RB as **P24_DATAPATH_0_RAM**

Guides and Tips:

- Add to the datapath a generic WF RAM as a new process. You will need modify the entity's ports. (Define the RAM as **2**ADDR_RAM_WIDTH x DATA_WIDTH**).
- The image in the next slide shows the block-diagram you should get.
- Two slides ahead there is a table containing the values to store in each memory position. Use signal initialization to store the data.

Adding a RAM to DATAPATH: architecture for designing

P24_Datapath_0_RAM

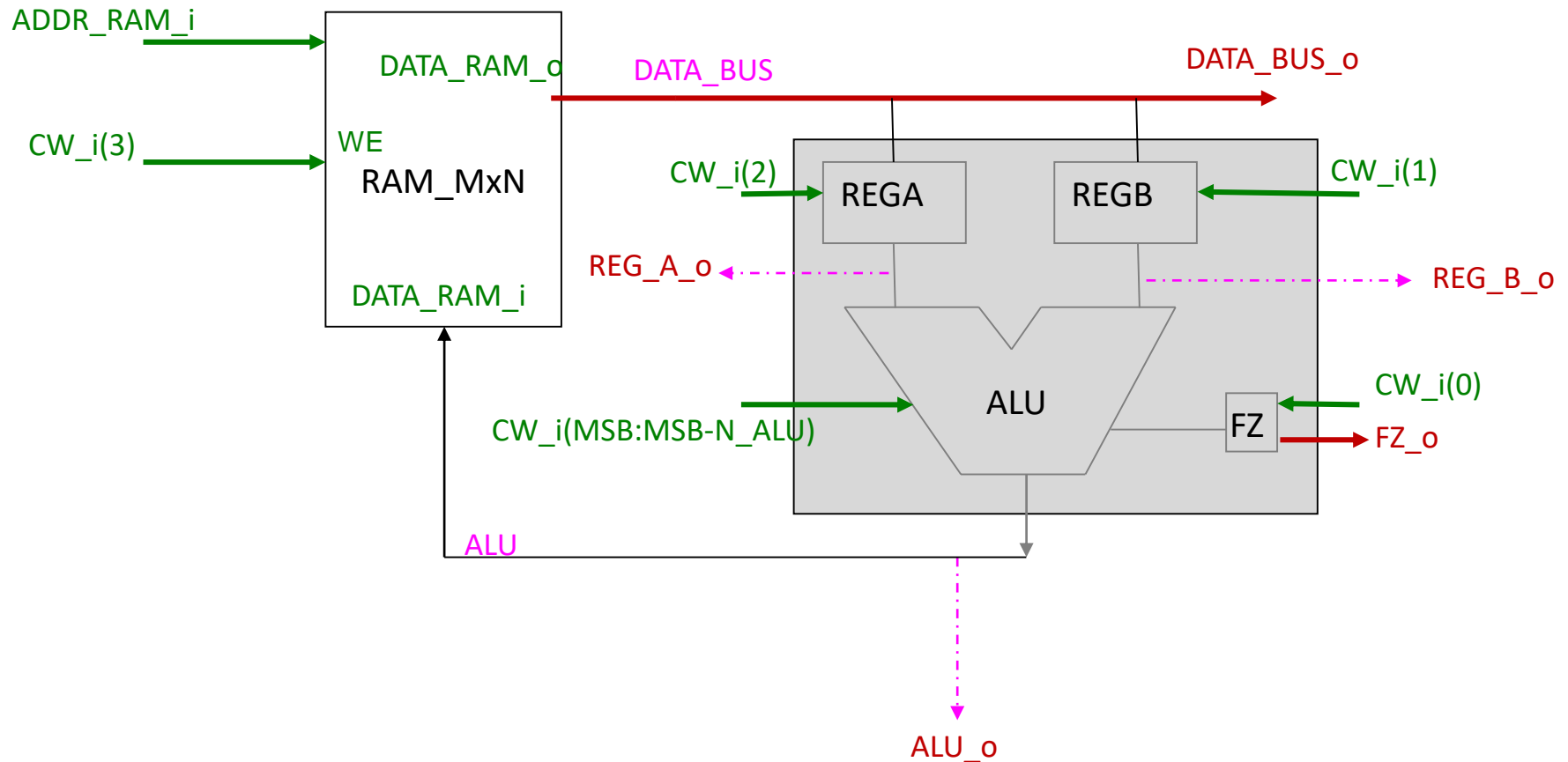

Adding a RAM to DATAPATH: initial values for the operands

Address (4bits) Hex.	Data (4 bits) Binary
0	0101
1	1111
2	1110
3	1110
4	1110
5	0000
6	0001
7	0010
8	0101
9	1111
A	0000
B	0000
C	0000
D	0000
E	0000
F	0000

The next slide shows the format to initialize a signal

Adding a RAM to DATAPATH: Initial values for RAM

First method :

Item 15th

```
signal RAM : ram_type:=("0000", "0001", "0010", "0011", "0000"  
, "1111", "0000", "0000", "0000"  
, "1111", "1100", "0011", "0010"  
, "0001", "0000", "0000");
```

Item 0th

Remember that the RAM is a
array of arrays data type.

Adding a RAM to DATAPATH: Initial values for RAM

Second method:

```
signal RAM: ram_type :=  
( 0 => "0001",  
  1 => "1111",  
  2 => "0101",  
  others => "0000");
```

Binary format

Index

Third method:

```
signal RAM: ram_type :=  
( 0 => X"1",  
  1 => X"F",  
  2 => X"5",  
  others => "0000");
```

Hexadecimal format

Remaining addresses
with the same value

Adding a RAM to DATAPATH: Initial values for RAM

Two options for “others” clause:

1.1. Set the value for each array in the matrix

```
RAM<=(others => "0000") ;
```

1.2. Set the value for each bit in the matrix

```
RAM<=(others => (others => '0')) ;
```

Adding a RAM to DATAPATH: Preparing the testbench

P24_Datapath_0_RAM: Add a testbench which writes the proper values for address and CW in each clock-cycle for each operation.

	MOV A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	<i>MOV operation, set B address RAM and update FZ</i>	00	1	0	0	1

-- 1) MOV A,B -----

-- CLK1: Read OPE_A in RAM(0)

```
ADDR_RAM_i  <= "0000";
```

```
CW_i        <= "000000";
```

```
wait for 10 ns;
```

-- CLK2: Load OPE_A

```
CW_i        <= "000100";
```

```
wait for 10 ns;
```

-- CLK3: Select ALU operation and FZ

```
-- Write result in RAM (3)
```

```
ADDR_RAM_i  <= "0011";
```


```
CW_i        <= "001001";
```

```
wait for 10 ns;
```

The readout is available
one clk-cycle after.

Adding a RAM to DATAPATH: Preparing the testbench

	MOV A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	MOV operation, set B address RAM and update FZ	00	1	0	0	1

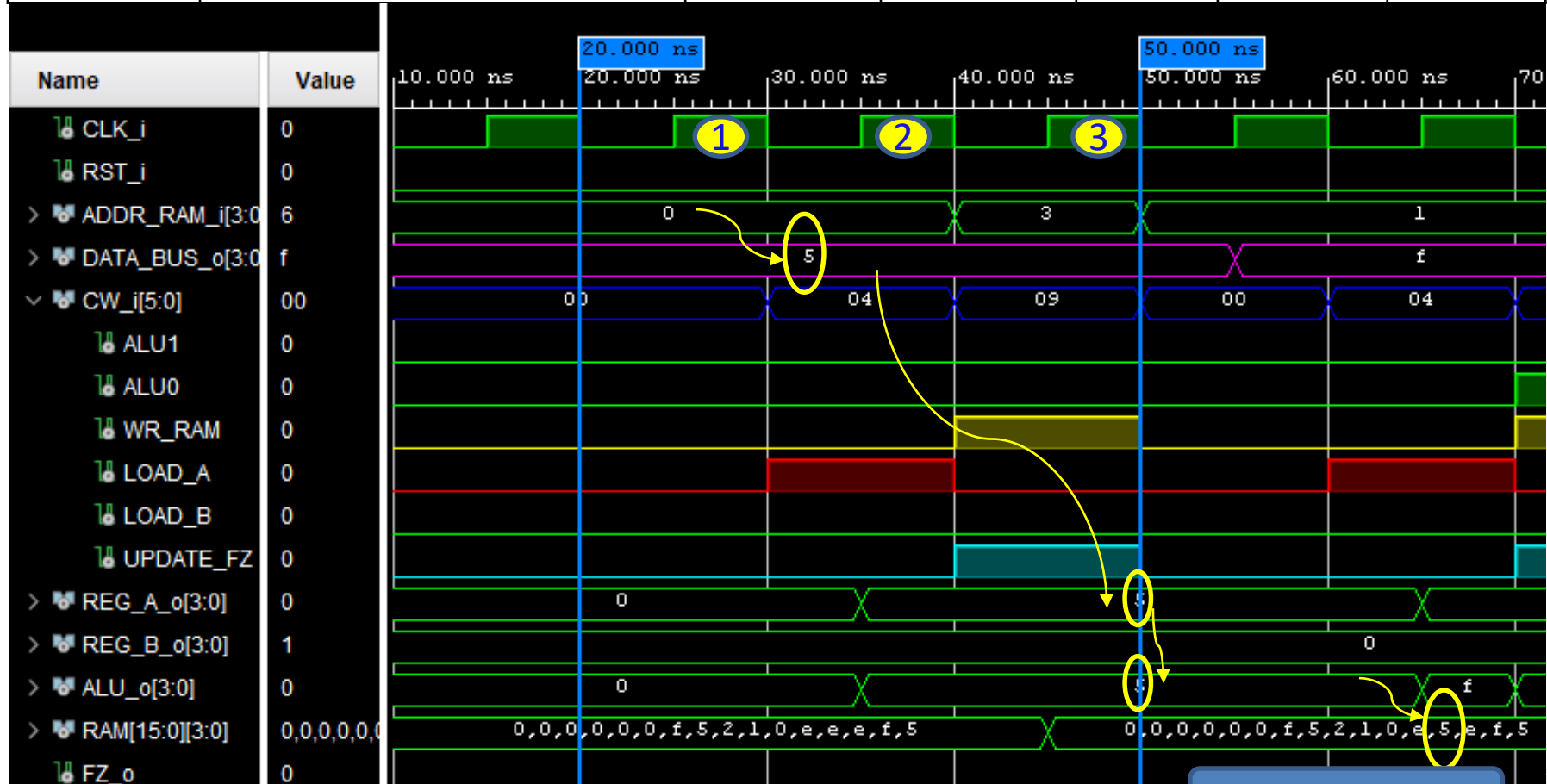

Addr 3 = 0x5

Adding a RAM to DATAPATH: Preparing the testbench

	INC A	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	INC operation and update FZ	01	1	0	0	1


```

-- 2) INC A-----
-
-- CLK1: Read OPE_A in RAM(1)
  ADDR_RAM_i  <= "0001";
  CW_i        <= "000000";
  wait for 10 ns;
-- CLK2: Load OPE_A
  CW_i        <= "000100";
  wait for 10 ns;
-- CLK3: Select OPE_ALU and FZ
  -- Write result in RAM(1)
  CW_i        <= "011001";
  wait for 10 ns;

```

Adding a RAM to DATAPATH: Preparing the testbench

	INC A	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	INC operation and update FZ	01	1	0	0	1

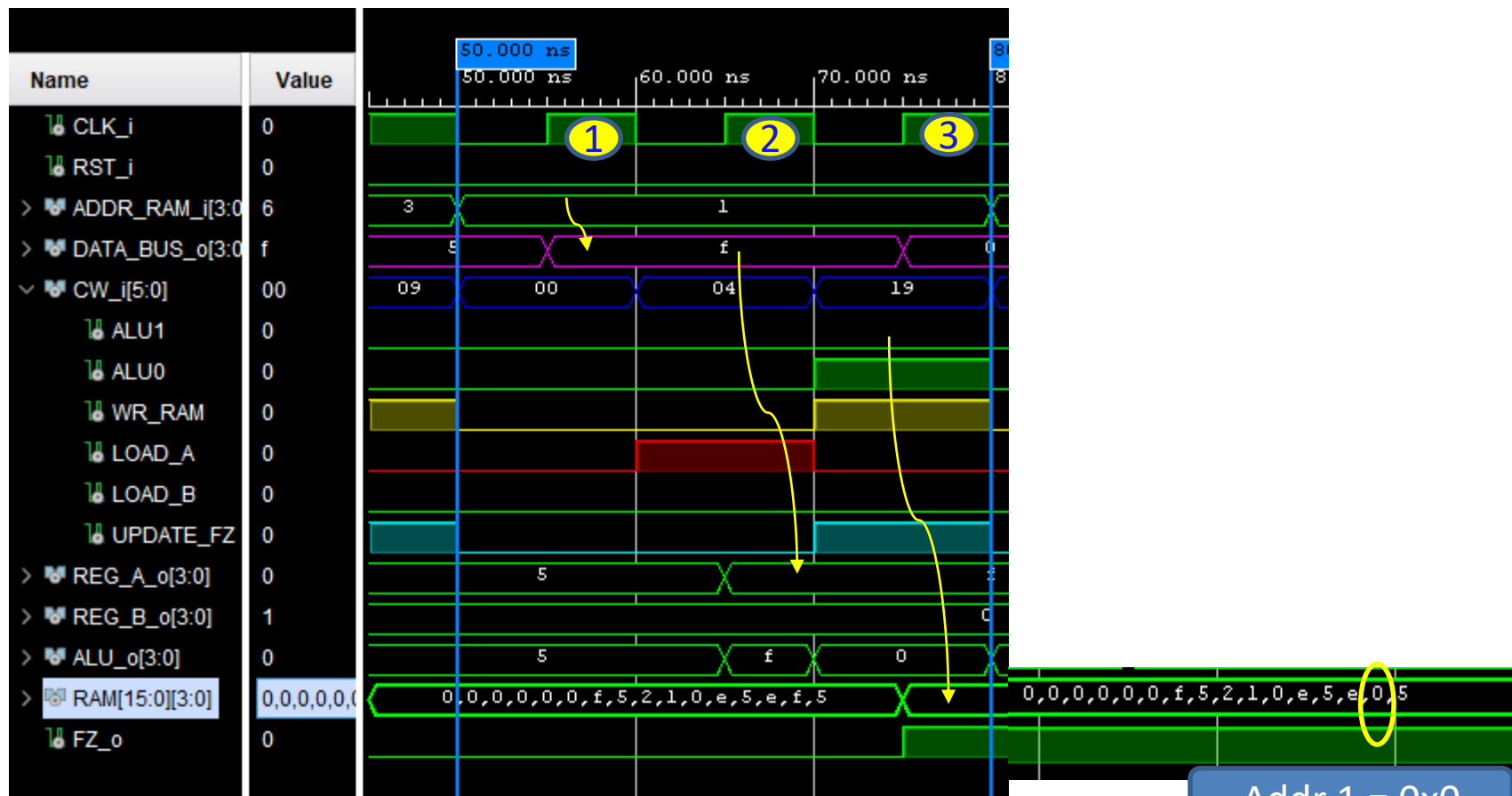

Addr 1 = 0x0

Adding a RAM to DATAPATH: Preparing the testbench

	ADD A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	<i>Load OPE_A</i>	00	0	1	0	0
3	Set RAM address (OPE_B)	00	0	0	0	0
4	<i>Load OPE_B</i>	00	0	0	1	0
5	<i>ADD operation and update FZ</i>	10	1	0	0	1


```

-- 3) ADD A,B-----
-- CLK1: Read OPE_A in RAM(3)
    ADDR_RAM_i  <= "0011";
    CW_i        <= "000000";
    wait for 10 ns;
-- CLK2: Load OPE_A
    CW_i        <= "000100";
    wait for 10 ns;
-- CLK3: Read OPE_B in RAM(4)
    ADDR_RAM_i  <= "0100";
    CW_i        <= "000000";
    wait for 10 ns;
-- CLK4: Load OPE_B
    CW_i        <= "000010";
    wait for 10 ns;
-- CLK5: Select OPE_ALU and FZ
    -- Write result in RAM(4)
    CW_i        <= "101001";
    wait for 10 ns;

```

Adding a RAM to DATAPATH: Preparing the testbench

	ADD A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	Set RAM address (OPE_B)	00	0	0	0	0
4	Load OPE_B	00	0	0	1	0
5	ADD operation and update FZ	10	1	0	0	1

 


Adding a RAM to DATAPATH: Preparing the testbench

	SUB A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	Set RAM address (OPE_B)	00	0	0	0	0
4	Load OPE_B	00	0	0	1	0
5	SUB operation and update FZ	11	1	0	0	1

```
-- 4) SUB A,B-----
-- CLK1: Read OPE_A in RAM(5)
    ADDR_RAM_i  <= "0101";
    CW_i        <= "000000";
    wait for 10 ns;
-- CLK2: Load OPE_A
    CW_i        <= "000100";
    wait for 10 ns;
-- CLK3: Read OPE_B in RAM(6)
    ADDR_RAM_i  <= "0110";
    CW_i        <= "000000";
    wait for 10 ns;
-- CLK4: Load OPE_B
    CW_i        <= "000010";
    wait for 10 ns;
-- CLK5: Select OPE_ALU and FZ
    -- Write result in RAM(6)
    CW_i        <= "111001";
    wait for 10 ns;
```

Adding a RAM to DATAPATH: Preparing the testbench

	SUB A,B	ALU_OP	WRITE_RAM	REG_A	REG_B	FZ
CLK	Micro-instructions	CW (4:3)	CW(3)	CW(2)	CW(1)	CW(0)
1	Set RAM address (OPE_A)	00	0	0	0	0
2	Load OPE_A	00	0	1	0	0
3	Set RAM address (OPE_B)	00	0	0	0	0
4	Load OPE_B	00	0	0	1	0
5	SUB operation and update FZ	11	1	0	0	1

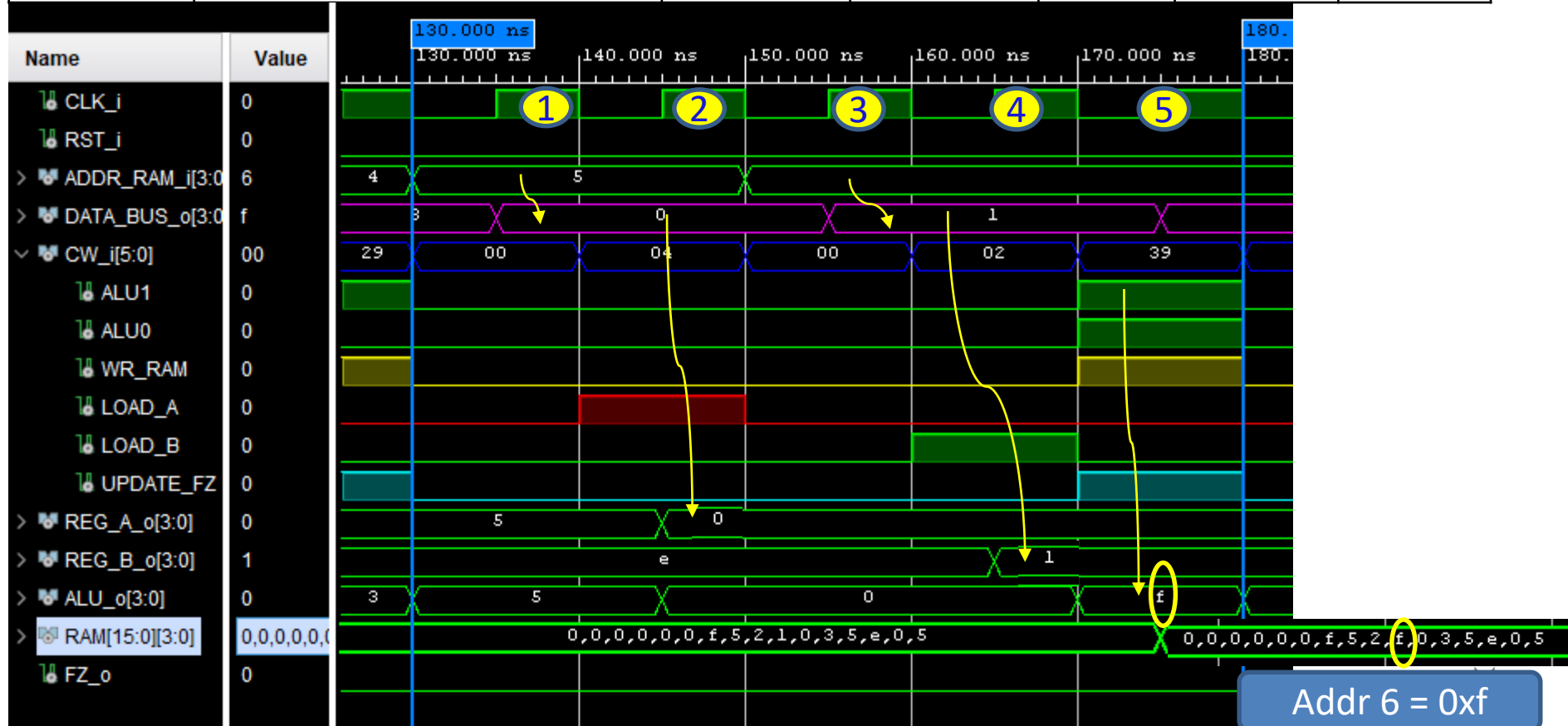

Addr 6 = 0xf


Adding a RAM to DATAPATH: the complete TB

- Add a testbench which sets the proper values for address and CW in each clock-cycle for each operation.

```
stimulus: process
begin
  CW_i      <= "000000";
  ADDR_RAM_i <= "0000";
  RST_i <= '1';
  wait for 10 ns;
  RST_i <= '0';
  wait for 10 ns;
-- 1) MOV A,B -----
-- CLK1: Read OPE_A in RAM(0)
  ADDR_RAM_i <= "0000";
  CW_i      <= "000000";
  wait for 10 ns;
-- CLK2: Load OPE_A
  CW_i      <= "000100";
  wait for 10 ns;
-- CLK3: Select ALU operation and FZ
  -- Write result in RAM (3)
  ADDR_RAM_i <= "0011";
  CW_i      <= "001001";
  wait for 10 ns;
```

```
-- 2) INC A-----
-- CLK1: Read OPE_A in RAM(1)
  ADDR_RAM_i <= "0001";
  CW_i      <= "000000";
  wait for 10 ns;
-- CLK2: Load OPE_A
  CW_i      <= "000100";
  wait for 10 ns;
-- CLK3: Select OPE_ALU and FZ
  -- Write result in RAM(1)
  CW_i      <= "011001";
  wait for 10 ns;
```

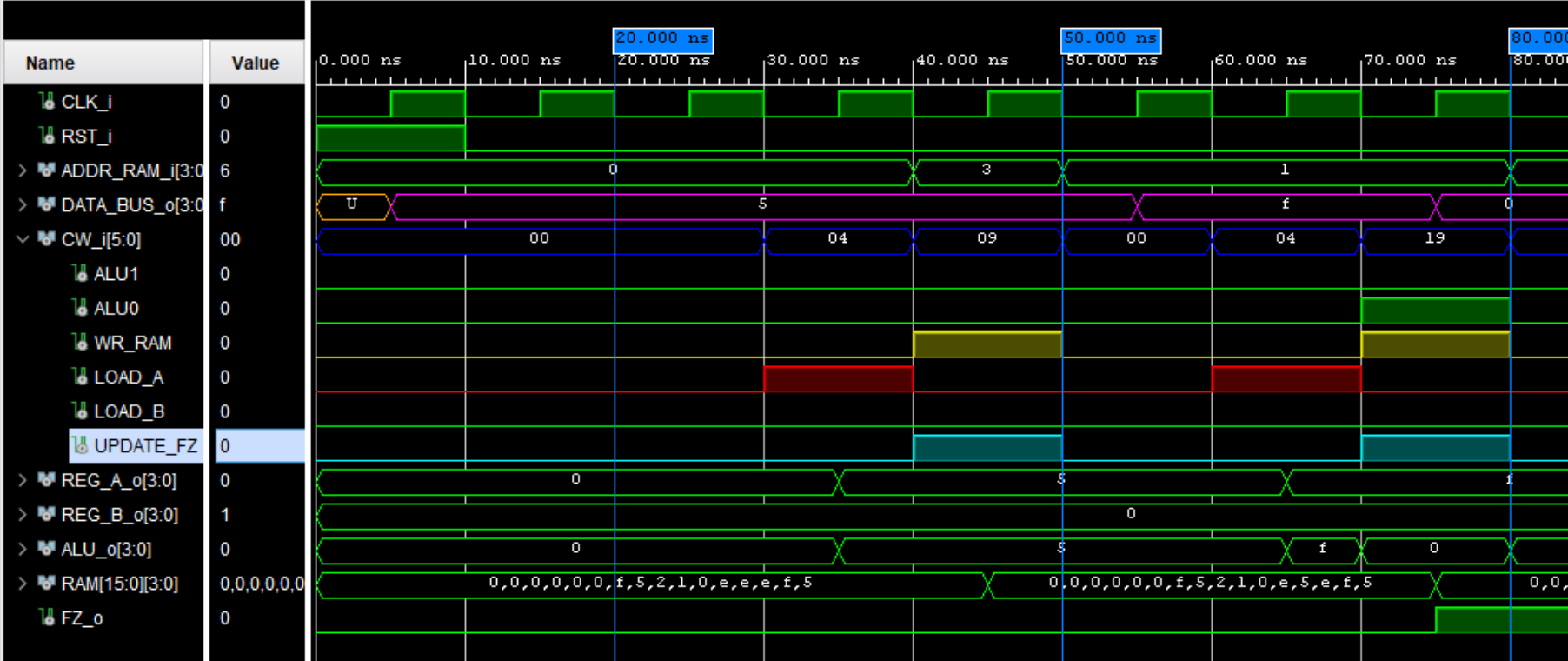Adding a RAM to DATAPATH: Complete simulation




Adding a RAM to DATAPATH

- Add a testbench which sets the proper values for address and CW in each clock-cycle for each operation.

```
-- 3) ADD A,B-----
-- CLK1: Read OPE_A in RAM(3)
  ADDR_RAM_i  <= "0011";
  CW_i        <= "000000";
  wait for 10 ns;
-- CLK2: Load OPE_A
  CW_i        <= "000100";
  wait for 10 ns;
-- CLK3: Read OPE_B in RAM(4)
  ADDR_RAM_i  <= "0100";
  CW_i        <= "000000";
  wait for 10 ns;
-- CLK4: Load OPE_B
  CW_i        <= "000010";
  wait for 10 ns;
-- CLK5: Select OPE_ALU and FZ
  -- Write result in RAM(4)
  CW_i        <= "101001";
  wait for 10 ns;
```

```
-- 4) SUB A,B -----
-- Read OPE_A in RAM(5)
  ADDR_RAM_i  <= "0101";
  CW_i        <= "000000";
  wait for 10 ns;
-- Load OPE_A
  CW_i        <= "000100";
  wait for 10 ns;
--- Read OPE_B in RAM(6)
  ADDR_RAM_i  <= "0110";
  CW_i        <= "000000";
  wait for 10 ns;
-- Load OPE_B
  CW_i        <= "000010";
  wait for 10 ns;
-- Select OPE_ALU and FZ
-- Write result in RAM(6)
  CW_i        <= "111001";
  wait for 10 ns;
  CW_i        <= "000000";
  wait for 10 ns;
```

Adding a RAM to DATAPATH

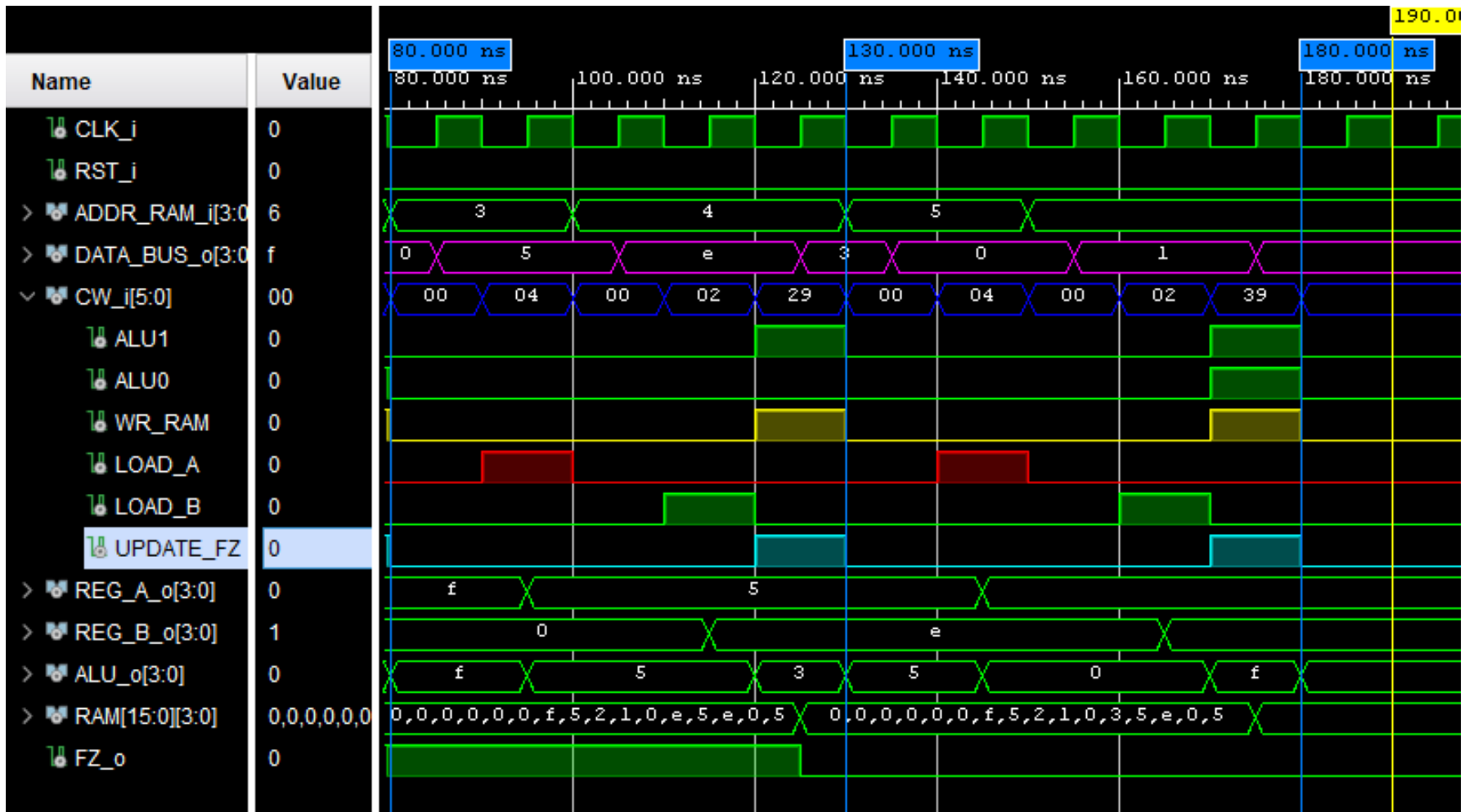

4.3. Adding a ROM (Program memory) to Didacomp


Adding a ROM memory (Program memory)

Create a new Project named **P25_DATA_PATH_0_ROM** and add one source called **"DATAPATH_0_ROM"**. Copy the code from the file in Project **"P24_DATAPATH_0_RAM"**. Then add the **ROM memory** (instructions), the **instruction register** and the **MUX** for selecting the address in the RAM (operands) as shown in the schematic.

Note: The schematic and the ROM contents are provided in the following slides

Adding ROM memory, instruction register and address RAM selection

P25_DATA_PATH_0_ROM

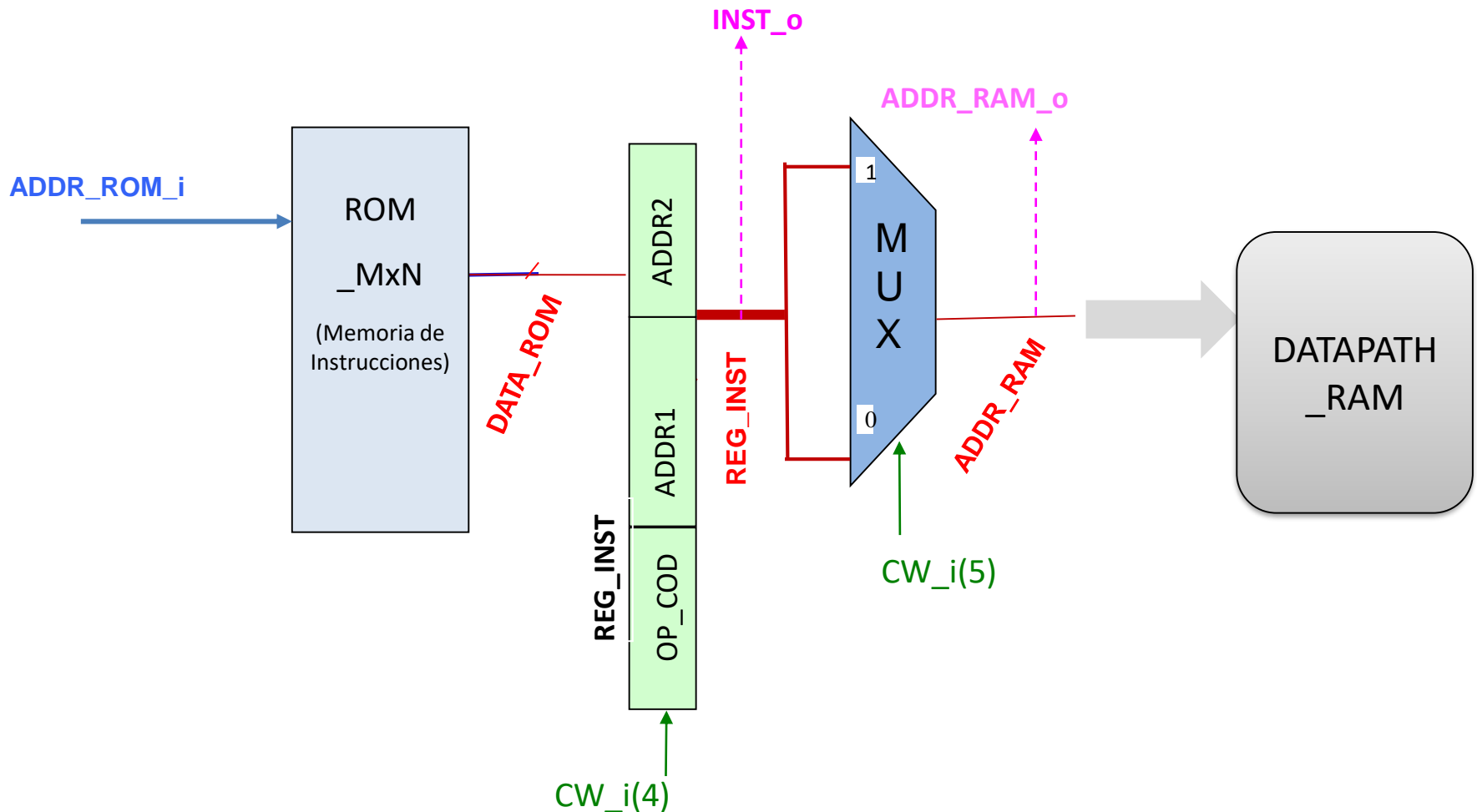

Contents of ROM memory

P25_DATA_PATH_ROM → ROM (instructions) contents

Dir. Hex	Instruction (12 bits)	Instruction functions
0	0010 1000 0011	ADD M[8],M[3] --> M[3]
1	0000 0001 0100	MOV M[1],M[4]
2	0001 0000 1001	INC M[0]
3	0011 0001 0001	SUB M[1],M[1] --> M[1] ; FZ=1
4	0100 0011 0111	BRZ [7] --> PC = 7
5	0000 0100 0000	
6	0010 0001 0010	
7	0010 0001 0010	ADD M[1],M[2] --> M[2]
8	0001 0000 0100	
...	0000 0000 0000	

Contents of ROM memory

P25_DATA_PATH_ROM

Add a testbench for checking the first instruction (Address 0x003) stored in the ROM program memory (SUB M[1],M[1] --> M[1]).

Tips:

- *You can base on the TB of the P24 Project (Lab_4 page 15). Take into account more bits are required for “**CW_i**”, and a new input, “**ADDR_ROM_i**” must be included instead of “**ADDR_RAM_i**”*
- *The needed stimuli for each CLK cycle is similar to that in the Bus control table written in “Tema 4_1_Diseño de un procesador: el camino de datos” (page 23). (Notice that in this case, **6 clk-cycles**, instead 5, are needed to complete the actions related to the SUB instruction. A different value must be applied to the ALU selection lines in CW_i).*

4.4. Entire microarchitecture of Didacomp

Entire microarchitecture of Didacomp


Create a new Project named **P26_DIDACOMP_uArq** and add one source called **“DATAPATH_0”**. Copy the code from the file **“Datapath_0”** (**P25_DATAPATH_0_ROM**). Then add the Program Counter (PC) and the jump structure as shown in the schematic.

Note: The values for the control Word (CW) are available in the lecture 4_1.

In the same file (**DATAPATH_0.vhd**) add the VHDL code to infer a second source to provide an address to ROM (instructions)

Estructura de salto de DidaComp

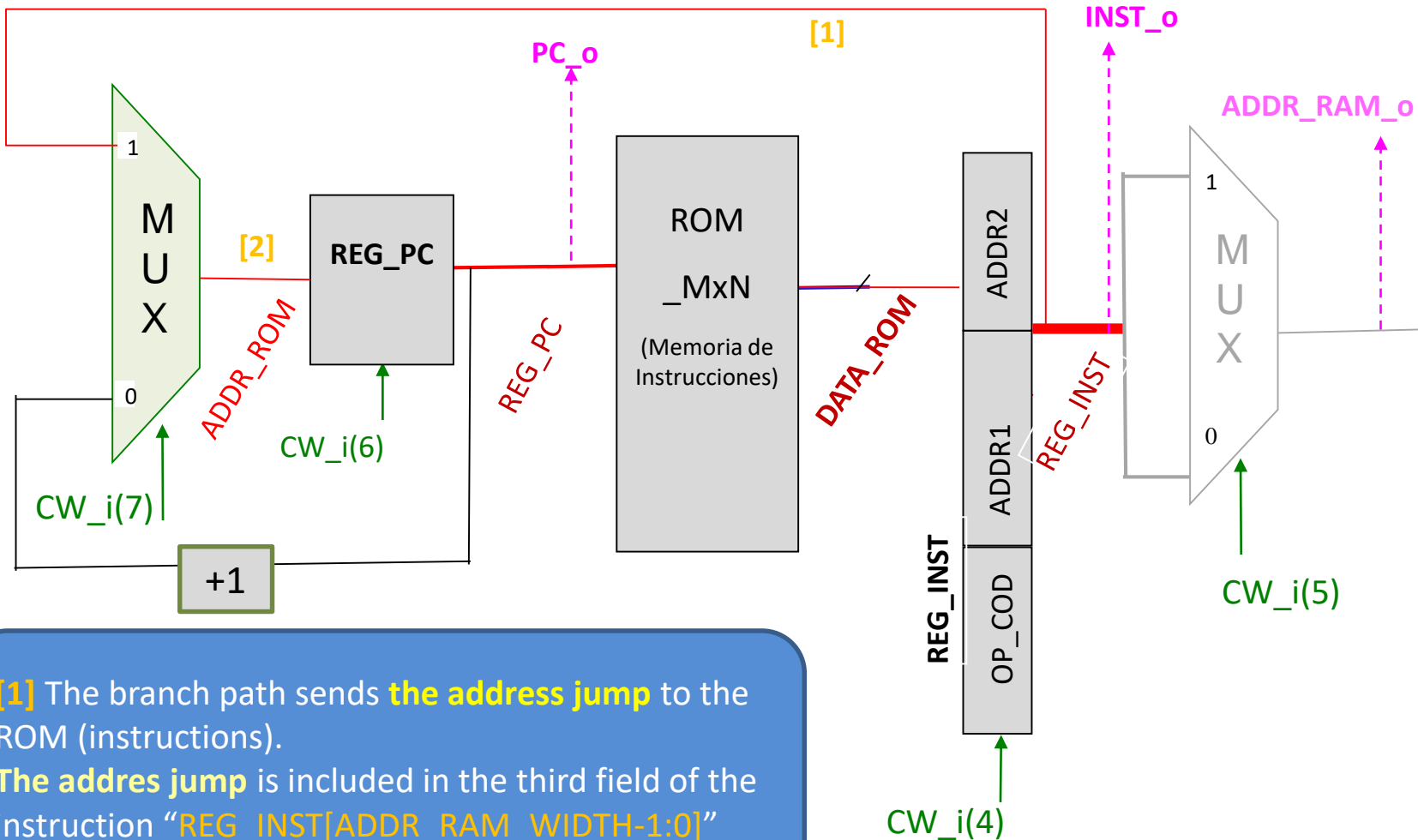
[2] Now, there are two sources of address for the ROM (instructions)



[1] The branch path sends **the address jump** to the ROM (instructions).
The address jump is included in the third field of the instruction "**REG_INST[ADDR_RAM_WIDTH-1:0]**"

Entire microarchitecture of Didacomp

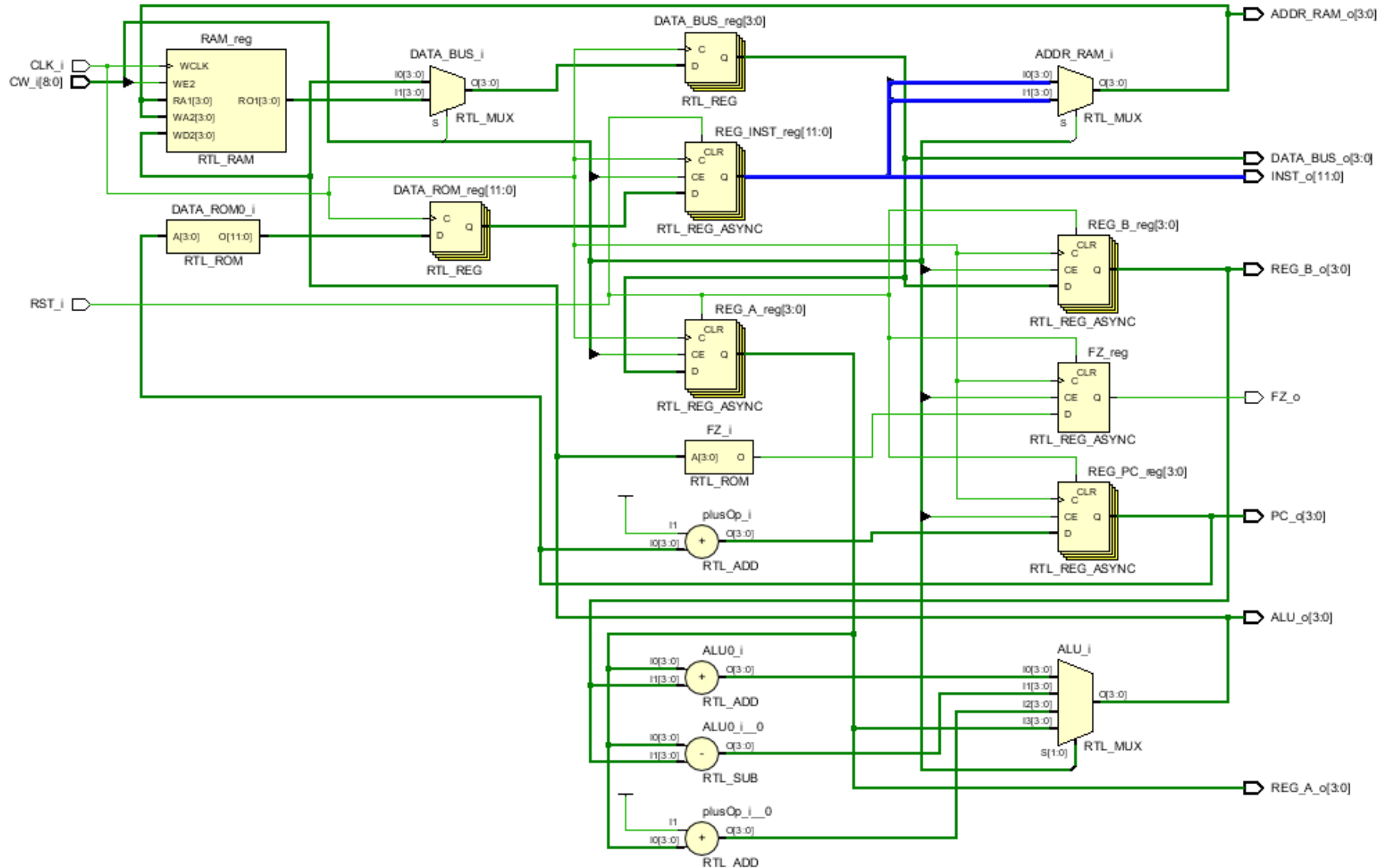Open the RTL Schematic and make sure you have something similar to the below image:



Didacomp microarquitectura

Create a new Project **P27_Didacomp_uArq_Nexys4**. Add a module called “**TOP**” to connect the “**DIDACOMP_uArq**” and “**Disp7Seg_8ON**”, to use the 7-segment displays to show the values in different points of Didacomp uArq.

- To avoid bouncing in the pushbuttons, add the component “**RISING_EDGE**”.
- In order to test the design onto **Nexys4**, add a constraints file to associate the ports with the below peripherals:

- Sw15-14 → **CW_i(9),CW_(8)** → **ALU**
- Sw3-0 → **CW_i(7), CW_i(5), CW_i(4), CW_i(3)**
- BTN → Down: **CW_i(6)** Left: **CW_i(2)**
Up: **CW_i(1)** Right: **CW_i(0)**
Central: **RST_i**

- Led 11-0 → **INST_o**
- Led 15 → **FZ_o**

- Display5 → **PC_o**
- Display4 → **ADDR_RAM_o**
- Display3 → **DATABUS_o**
- Display2 → **REG_A_o**
- Display1 → **REG_B_o**
- Display0 → **ALU_o**

- Do not forget to add the clock constraint.

Microarquitectura de Didacomp

Check the design in Nexys4 executing the whole program contained in the ROM and therefore testing the complete ISA.

TIP: In order to help you to recall the function of each switch or button, you may write the functions in a paper and to place it below the peripherals.



REG_INST
R/W